

UHF TV- modulator

We use the term 'modulator' as a conveniently short way to describe a circuit comprising an r.f. oscillator and an amplitude modulator (figure 1). In many simple modulator circuits the oscillator and modulator are but a single transistor, the video signal being injected direct into the base of the oscillator transistor to vary the amplitude of oscillation. The disadvantage of this method is that the frequency stability of the oscillator suffers, and phase or frequency modulation can also be introduced, which is apparent as poor picture definition. Ideally, the oscillator output amplitude should remain constant, and modulation should be performed by feeding the signal through a separate modulator circuit.

Many simple TV modulators have an oscillator frequency whose fundamental lies in the VHF band, since these are the highest frequencies that can be obtained using conventional construction techniques (wound coils). For reception in the UHF band on which modern TV's operate, one has to rely on the large harmonic content of the oscillator, which is not an entirely satisfactory solution.

A modulator whose fundamental lies in the UHF band has significant advantages over a VHF modulator:

- when used with equipment containing logic circuits (pattern generators for example) a UHF modulator is much less prone to spurious interference.
- the circuit can be simply constructed using striplines etched on a p.c. board instead of conventional wound inductors.
- a large number of channels are available in the UHF band, so that even with fairly generous component tolerances the oscillator frequency will still lie in the correct band.

The spectrum of a normal amplitude modulated signal consists of the carrier signal and two sidebands, one above and one below the carrier frequency, each occupying a bandwidth equal to the bandwidth of the modulating signal. Thus a signal amplitude modulated with video information having a 5.5MHz

Circuits which produce an amplitude modulated VHF or UHF signal from a video input signal have many applications. They allow direct connection to the TV aerial input of such devices as TV games, video biofeedback circuits and test pattern generators, to name but a few. Unfortunately, the performance of most simple modulators leaves much to be desired. However, the circuit described in this article, though extremely simple (one transistor!), offers extremely good performance.

bandwidth (standard I), would occupy a channel width of 11MHz.

However, each of the sidebands contains all the information present in the modulating signal, so one of the sidebands is redundant. To allow the maximum number of channels to be packed into the UHF band, the channel width is limited to 8 MHz, and in broadcast TV transmitters this is achieved by the use of a sideband filter, which partially suppresses the lower sideband to produce the type of spectrum illustrated in figure 2.

The lower sideband is not totally suppressed, nor is the carrier suppressed as in a true SSB transmission, since this would require a complex SSB demodulator in the TV receiver, whereas partial sideband suppression and retention of the carrier allows a simple envelope demodulator to be employed.


However, since the modulator described in this article is not intended for broadcast purposes, but merely as an interface between video signals and the TV set, suppression of the unwanted sideband is not necessary. Perfectly satisfactory results will be obtained by tuning the TV set to the 'correct' sideband.


The circuit

Figure 3 shows the complete circuit of the UHF modulator, which consists of two sections. The UHF oscillator section is constructed around T1 and stripline inductors L1 and L3. The oscillator frequency may be tuned over the range of approximately 430 MHz to 600 MHz by means of C6.

Stripline L2 is inductively coupled to L1 and thus picks up part of the UHF signal from the oscillator. Trimmer C7 allows L2 to be tuned to the same frequency as the oscillator.

Diode D1 functions as a current controlled resistor; in the absence of a video input signal its dynamic forward resistance is high. If a positive voltage is applied to the video input then the current through the diode will increase and its dynamic resistance will fall, thus damping the resonant circuit L2/C7 and attenuating the signal developed across L2. With potentiometer P1 set to maximum the modulator will saturate at an input voltage of approximately 2

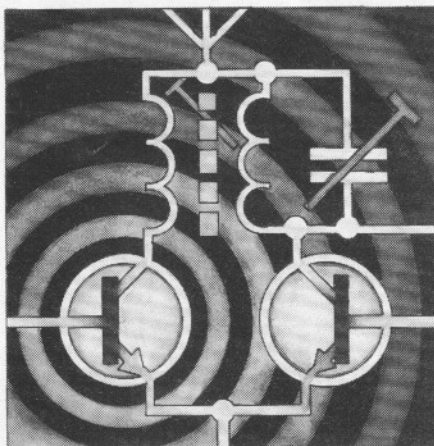

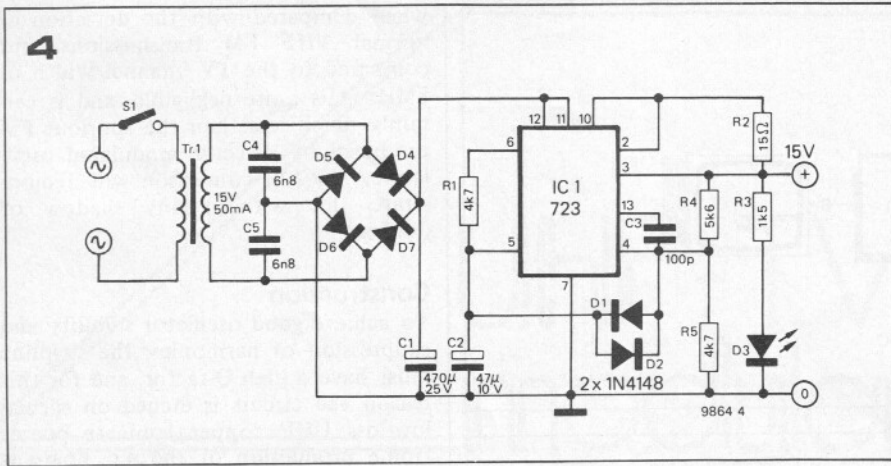

Parts list to figure 3

Resistors:

- R1 = 100 Ω
- R2, R3 = 3k9
- P1 = 10 k preset
- P2 = 1 k preset

Capacitors:

- C1 = 3p3
- C2 = 150 p
- C3 = 47 μ/25 V
- C4 = 100 n
- C5 = 6p8
- C6, C7 = trimmer 1.5 - 5 p

Semiconductors:

- T1 = FET E 310
- D1 = 1N4148

Miscellaneous:

- L1, L2, L3 = striplines on p.c. board.

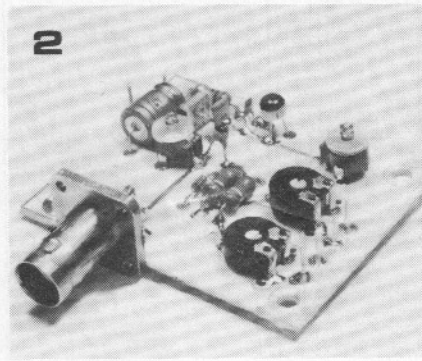
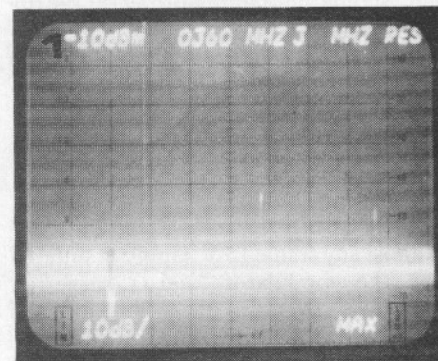
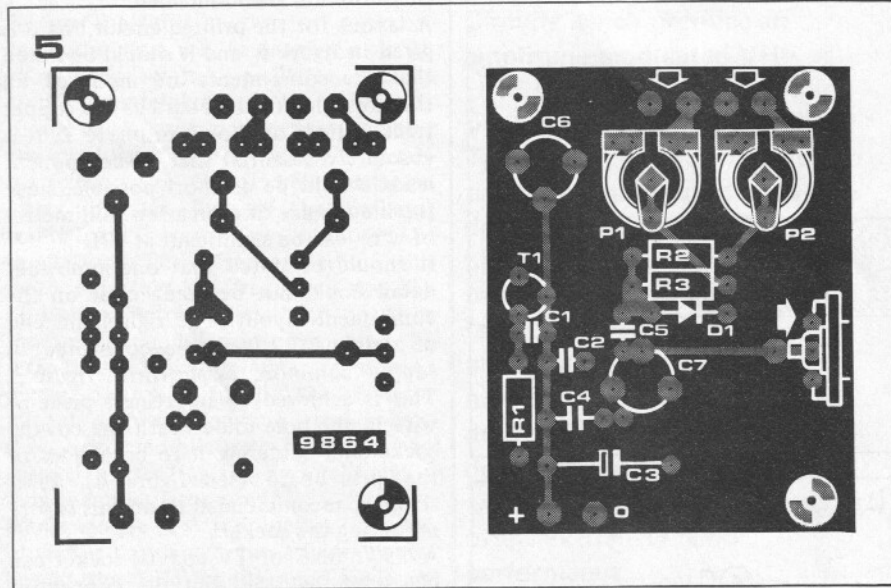



Figure 4. Suggested power supply circuit for the modulator. This can be mounted on the p.c. board EPS 9499-2.

Figure 5. Printed circuit board and component layout for the UHF TV modulator (EPS 9864).

Figure 6. Note the (arrowed) connection between the 'cold' end of L2 and supply common.

Photo 1. This spectrum analyser trace illustrates the purity of the UHF oscillator signal.

Photo 2. The completed modulator board.

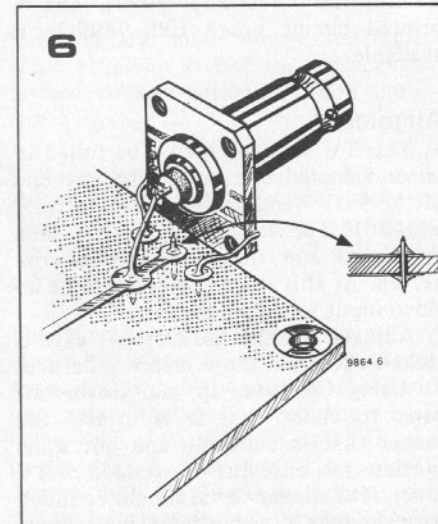

the effect of C6 is quite coarse the final fine tuning to the carrier signal should be carried out with the TV tuning controls. As a rough guide C6 should be approximately in its mid-position (vanes half-closed) when the oscillator is tuned somewhere between channels 21 and 30.

4. Set the wiper of P1 to its mid-position and feed in a video signal of a few volts peak-to-peak. Adjust the TV tuning controls until a sharply defined picture is obtained, although at this stage it may not sync properly.

5. Turn down P1 until the picture is barely visible, or until it goes out of sync if originally in sync.

6. Adjust C7 for maximum contrast, and finally turn up P1 until the desired contrast range is obtained in the picture. This completes the alignment.

Performance

Photo 1 shows a spectrum analyser trace of the unmodulated carrier signal. The negative marker pulse at the left of the screen is at 360 MHz, whilst just less than one division to the right (at about 500 MHz) the fundamental of the carrier signal can be seen. The horizontal scale is 180 MHz/division. The vertical scale is 10 dB/division, with the top of the screen being at -10 dBm with respect to 0 dBm = 100 mV. The top of the screen thus represents an amplitude of 70 mV. The second and third harmonics are extremely attenuated, about 53 dB below 0 dBm in the case of the second harmonic and 56 dB down in the case of the third harmonic. These figures represent absolute signal levels of around 225 μV for the second harmonic, and 160 μV for the third harmonic. The amplitude of the fundamental is certainly not small; as can be seen from the photograph it extends off the top of the trace beyond the -10 dBm (70 mV) level.

Editorial note: FCC regulations prohibit the use of home-built TV modulators in the U.S.A.